

Quiz 5

1. What is the minimum number of flip flops to count from 20 to 8 ?

A. 3 B. 4 C. 5 D. 6

The answer is 4 as there are 11 states from 20 to 8. A flip-flop is a register that can store one bit value. We need 11 states so $2^4 \geq 11$ is the final answer

2. Given a 120 MHz clock and the following module to slow the clock down. What is the frequency of the new clock.


```
1
2
3  module slow_clkgen (input clk, rst, sel, output clk_out);
4
5      reg [23:0] counter;
6
7      always @(posedge clk)
8      begin
9          if (rst)
10             counter <= 23'd0;
11          else
12             counter <= counter + 1'b1;
13      end
14
15      assign clk_out = counter[22];
16
17  endmodule
```

This question is short answer. Be careful if the question asks period instead of frequency

$$120 \text{ MHz} = 120 \cdot 10^6 \text{ Hz}$$

$$\text{Answer: } \frac{120 \cdot 10^6}{2^{23}} = 14,3 \text{ Hz} = \frac{1}{14,3} \text{ s period}$$

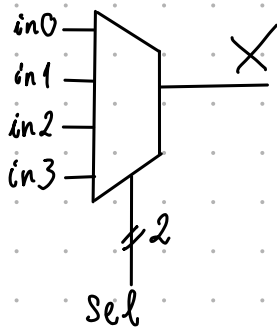3. Given a multiplexer with this following design.



With a assigned to sel 0 and b is assigned to sel 1. What is the value of $in0, in1, in2, in3$ if we have this boolean expression:

$$f(a, b, c) = \sum m(2, 4, 5, 7)$$

K-map:

		ab			
		00	01	11	10
c	0	0	1	0	1
	1	0	0	1	1

$$ab = 00 \rightarrow 0$$

$$ab = 01 \rightarrow c'$$

$$ab = 10 \rightarrow 1$$

$$ab = 11 \rightarrow c$$

So the answer is $0, c', 1, c$

4. What are the gates that yield output = 1 when all inputs are 0

XNOR, NOR, NAND

5. A SR-Latch built with a pair of 2-input NOR gate has active high inputs S and R?

True

False

SR Latch NOR \Rightarrow active high
NAND \Rightarrow active low

6. Given a Verilog assignment

assign res = $a \& \& b \parallel !a \& \& c ? a \& \& c : !b \parallel !c$

$!b \parallel !c$

With $a=0, b=1, c=1$. What is the output of res

$$res = \frac{a \& \& b}{0} \parallel \frac{!a \& \& c}{1} ? \frac{a \& \& c}{0} : \frac{!b \parallel !c}{1}$$




1 ? 0 1

0 0 0

7. Non-blocking assignment should always be in a Sequential always

True False

8. In what condition makes the Q to be 1

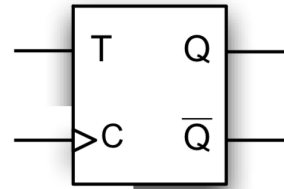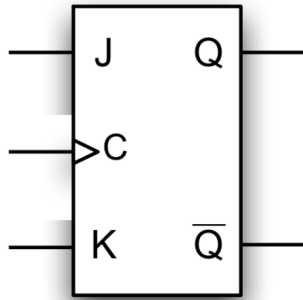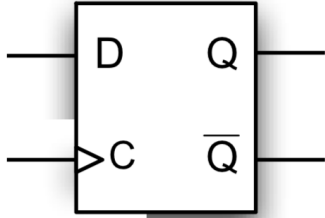

a) $D=0$

b) $J=1; K=1$

c) $J=1; K=0$

d) $J=1$